

Equivalent Circuit Model

Ning Tian

10/27/2020

1 Thevenin Model

1.1 $I > 0$ for charge

$$\begin{cases} \dot{x} = Ax + Bu & (1a) \\ y = \text{OCV}(\text{SoC}) + V_1 + V_2 + R_0u & (1b) \end{cases}$$

$$A = \begin{bmatrix} 0 & 0 & 0 \\ 0 & -\frac{1}{R_1C_1} & 0 \\ 0 & 0 & -\frac{1}{R_2C_2} \end{bmatrix}, \quad B = \begin{bmatrix} \frac{1}{3600Q_c} \\ \frac{1}{C_1} \\ \frac{1}{C_2} \end{bmatrix}, \quad x = \begin{bmatrix} \text{SoC} \\ V_1 \\ V_2 \end{bmatrix}, \quad u = I$$

1.2 $I > 0$ for discharge

$$\begin{cases} \dot{x} = Ax + Bu & (2a) \\ y = \text{OCV}(\text{SoC}) - V_1 - V_2 - R_0u & (2b) \end{cases}$$

$$A = \begin{bmatrix} 0 & 0 & 0 \\ 0 & -\frac{1}{R_1C_1} & 0 \\ 0 & 0 & -\frac{1}{R_2C_2} \end{bmatrix}, \quad B = \begin{bmatrix} -\frac{1}{3600Q_c} \\ \frac{1}{C_1} \\ \frac{1}{C_2} \end{bmatrix}, \quad x = \begin{bmatrix} \text{SoC} \\ V_1 \\ V_2 \end{bmatrix}, \quad u = I$$

2 Nonlinear Double-Capacitor Model

2.1 $I > 0$ for charge

$$\begin{cases} \dot{x} = Ax + Bu & (3a) \\ y = h(V_s) + V_1 + R_0u & (3b) \end{cases}$$

$$A = \begin{bmatrix} -\frac{1}{C_b(R_b+R_s)} & \frac{1}{C_b(R_b+R_s)} & 0 \\ \frac{1}{C_s(R_b+R_s)} & -\frac{1}{C_s(R_b+R_s)} & 0 \\ 0 & 0 & -\frac{1}{R_1C_1} \end{bmatrix}, \quad B = \begin{bmatrix} \frac{R_s}{C_b(R_b+R_s)} \\ \frac{R_b}{C_s(R_b+R_s)} \\ \frac{1}{C_1} \end{bmatrix}, \quad x = \begin{bmatrix} V_b \\ V_s \\ V_1 \end{bmatrix}, \quad u = I$$

2.2 $I > 0$ for discharge

$$\begin{cases} \dot{x} = Ax + Bu & (4a) \\ y = h(V_s) - V_1 - R_0 u & (4b) \end{cases}$$

$$A = \begin{bmatrix} -\frac{1}{C_b(R_b+R_s)} & \frac{1}{C_b(R_b+R_s)} & 0 \\ \frac{1}{C_s(R_b+R_s)} & -\frac{1}{C_s(R_b+R_s)} & 0 \\ 0 & 0 & -\frac{1}{R_1 C_1} \end{bmatrix}, \quad B = \begin{bmatrix} -\frac{R_s}{C_b(R_b+R_s)} \\ \frac{R_b}{C_s(R_b+R_s)} \\ \frac{1}{C_1} \end{bmatrix}, \quad x = \begin{bmatrix} V_b \\ V_s \\ V_1 \end{bmatrix}, \quad u = I$$